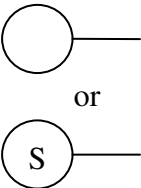
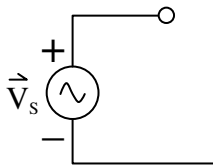
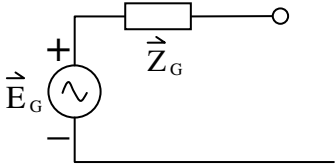
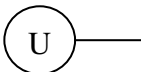
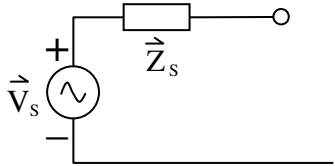
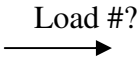
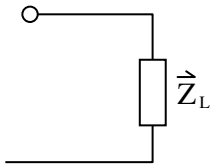
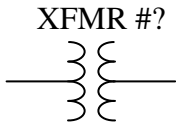
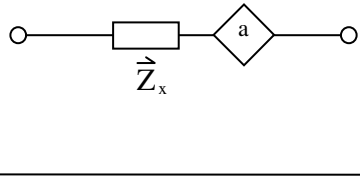
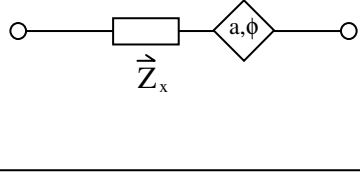
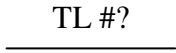
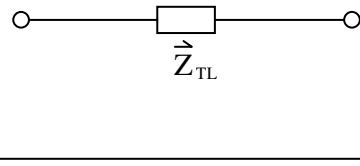


Device	One Line Diagram	Equivalent Circuit
Ideal Source (Infinite Bus)		
Generator		
Electric Utility Tie		
Load		
1ϕ XFMR		
3ϕ XFMR	same as above	
TL or Power Cable (Series Impedance Model)		
TL or Power Cable (Pi-Model)	same as above	