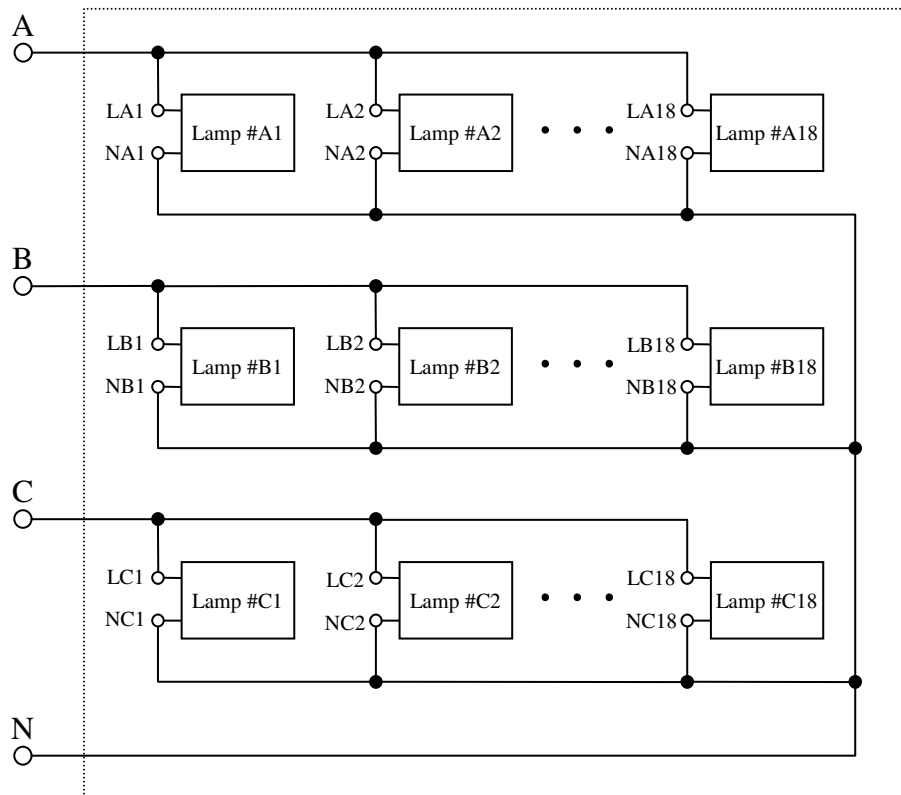


Part 4 Solution

Draw a **wiring diagram** for one of the lighting arrays. Use ditto (...) notation instead of drawing each of the 54 individual lamps.



Part 5 Solution

Draw an **equivalent circuit** for the **entire power system**. Use the series impedance model for all of the power cables in the system.

